

Chapter-7

Module - 2

Prof. H. M. Prasad M.Tech.
Assistant Professor of EEE
Concordia Institute of Technology
K. I. T. A. Hall, Bengaluru - 560 036.

OP-AMP's and its Applications

(1)



Define op-amp ?

Op-amp is a directly coupled multistage voltage amplifier with high gain. It has very high input impedance and very low output impedance.

Op-amps are used for performing mathematical operations such as addition, subtraction, multiplication, integration and differentiation.

NOTE :- The op-amp is used to perform various mathematical operations. Thus it is called operational amplifier.

Pin diagram and op-amp symbol.

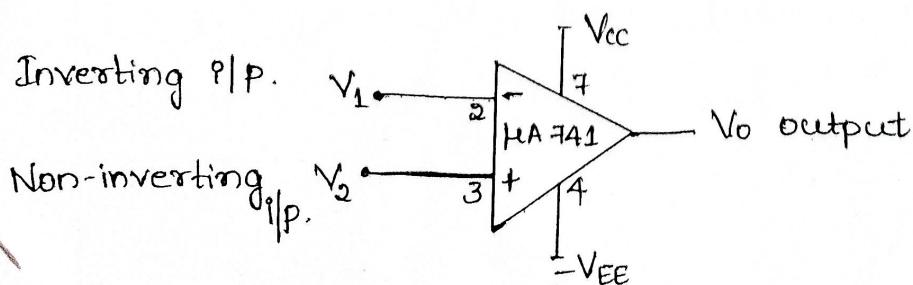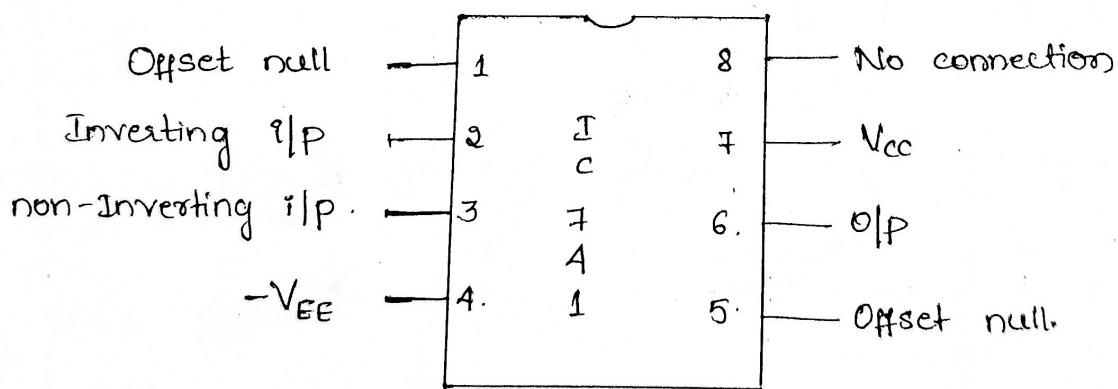

- V_1 is the voltage at the inverting input.
 V_2 is the voltage at the non-inverting input.
 V_o is the output voltage.
- * The o/p voltage V_o is proportional to the difference between the i/p voltage.
 i.e $V_o = A(V_2 - V_1)$
 - Where A is the open-loop voltage gain.

Inverting modes:-

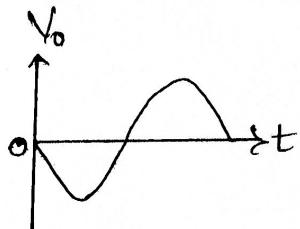
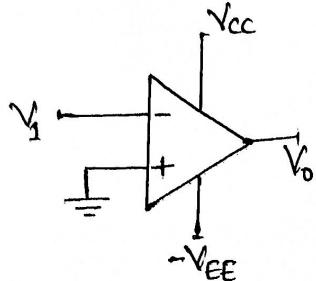
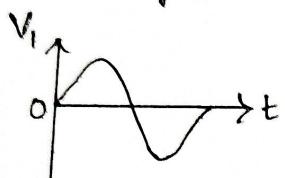


fig 1: Inverting amplifier.

- * In inverting mode i/p is applied to the inverting terminal and non-inverting terminal is grounded.
- * The amplified voltage is 180° out of phase with respect to applied i/p voltage.

$$\text{i.e } V_o = -AV_1.$$

NOTE :- Negative sign indicates that o/p is 180° out of phase.

Non-Inverting modes:-

In non-inverting mode, i/p is applied to the non-inverting terminal and inverting terminal is grounded.

(2)

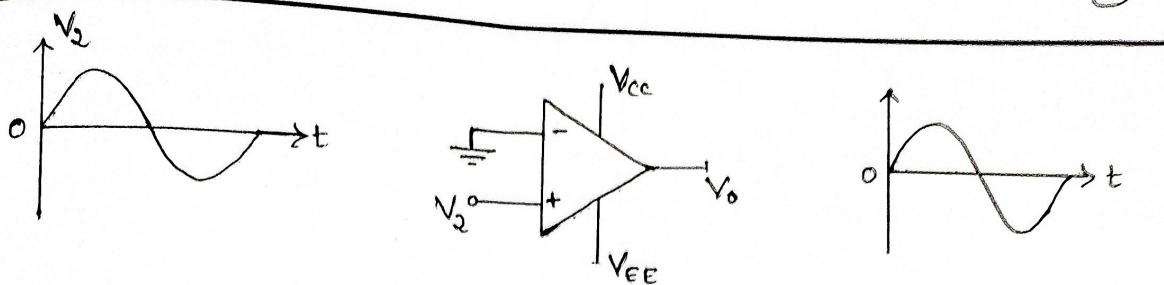


fig 2 :- Non-Inverting amplifier.

- * The amplified o/p voltage is in phase w.r.t to applied i/p voltage.
i.e. $V_o = A V_2$.

Block-diagram of op-amp :-

Draw the block schematic of an op-amp and explain the function of each stage.

June - 04, 6M

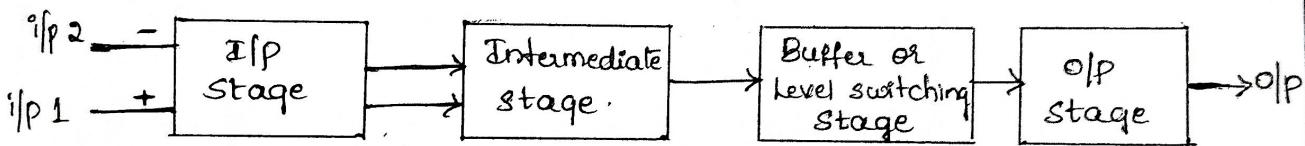


fig 1 :- Block diagram of op-amp.

Input stage :-

The op-amp has two i/p terminals. Its o/p stage requires dual i/p terminals with high i/p impedance. These requirements are satisfied by the dual i/p balanced o/p differential amplifier.
[Two i/p's & two o/p's].

Its function is to amplify the difference between the two i/p signals. It provides high differential gain, high i/p impedance and low o/p impedance.

Intermediate stage :-

The overall gain requirement of an op-amp is very high, since the i/p stage alone cannot provide such a high gain. The main function of the intermediate stage is provide such a high gain.

It consist of another differential amplifier with the dual i/p unbalanced o/p (single ended). Practically the intermediate stage is chain of cascaded amplifiers called as multistage amplifiers are used.

Buffer and level shifting stage :-

In intermediate stage all amplifiers are directly coupled. In the absence of coupling capacitors, DC voltage level gets amplified. Such a high dc level may drive the transistor into saturation. It causes distortion.

The level shifting stage brings the DC level to ground (zero).

O/P stage :- The o/p stage require low o/p impedance large voltage swing. This is satisfied by class B push pull emitter follower circuit.



Ideal characteristics :-

- * List the important characteristics of an ideal op-amp.
- * Explain the term op-amp. List the characteristics of an ideal op-amp.
- * Describe an op-amp and its important characteristics.

* What are the characteristics of an Ideal op-amp.

Jan - 03, 5 M

Jan - 08, 6 M

Dec - 10, 6 M

July - 03, 4 M

July - 08, 6 M

Jan - 11, 8 M.

Jan - 04, 4 M

Jan - 10, 4 M

Jan - 07, 6 M.

July - 09, 4 M

Op-amp is direct coupled multistage voltage amplifier with very high gain. It has very high i/p impedance and a very low o/p impedance.

The ideal characteristics of op-amp are:-

1. Infinite voltage gain ($A_{OL} = \infty$) :-

The gain loop voltage gain (A_{OL}) of the ideal op-amp is very large infinity.

$$A_{OL} = \infty.$$

2. Infinite i/p impedance [$R_i = \infty$] :-

An ideal op-amp does not draw any current from the voltage source connected to its i/p terminals. Thus its o/p impedance is infinite.

$$\text{i.e. } R_{in} = \infty.$$

3. Zero output impedance [$R_o = 0$] :-

The o/p voltage of an ideal op-amp is independent of the current drawn from it. This means op-amp has zero o/p impedance. It is infinite.

$$\text{i.e. } R_{out} = \infty, \text{ i.e. } R_o = 0.$$

4. Infinite Bandwidth ($BW = \infty$) :-

An ideal op-amp amplifies signals of any frequency with a constant gain, which implies that op-amp has infinite BW i.e. $BW = \infty$.

5) Infinite CMRR [$P = \infty$] :-

[CMRR is defined as the ratio of differential voltage gain to common mode voltage gain.
i.e. $CMRR = P = \frac{A_d}{A_c}$]

The common mode rejection ratio of an ideal op-amp is infinite i.e. $CMRR = \infty$.

6) Infinite slew rate [$SR = \infty$] :-

An ideal op amp has infinite slew rate
this implies that the o/p voltage changes simultaneously with the i/p voltages.

7) The characteristics of an ideal op-amp do not change with temperature.

8) The power supply rejection ratio of an ideal op-amp is zero. i.e. $PSRR = 0$.

9) Zero offset voltage :-

The presence of small o/p voltage when $V_1 = V_2 = 0$ is called an offset voltage.

For an ideal op-amp offset voltage is zero.

* Define and mention the importance of the following terms with respect to op-amp.

- i) CMRR ii) Slew rate iii) PSRR
iv) IIP offset voltage.

July - 05, 10M

* Define and explain briefly the following terms with respect to op-amp.

(4)

- i) O/P offset voltage ii) CMRR iii) SVRR iv) Slew Rate.

Jan - 06, 10M

* Define the term slew rate and CMRR of an op-Amp and mention their typical values for 741 op-amp.

i) CMRR :-

CMRR is defined as the ratio of the differential gain 'Ad' to the common mode gain 'Ac'.

$$\text{CMRR} = \rho = \frac{A_d}{A_c}$$

CMRR is always expressed in decibels as

$$(\text{CMRR})_{\text{dB}} = 20 \log_{10} \frac{A_d}{A_c}$$

The typical value of CMRR for 14741 op-amp is 90 dB.

ii) Slew Rate :-


Slew rate of the op-amp is defined as the maximum rate of change of its o/p voltage w.r.t time & is expressed in volts per microsecond.

$$SR = \frac{dV_o}{dt} \Big|_{\text{max.}} \text{ V/msec.}$$

For 741. SR = 0.5 V / μsec.

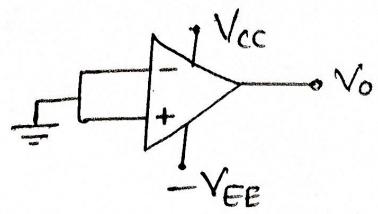(iii) O/p offset voltage :-

When both the IIP terminals are shorted and connected to ground, the o/p should be ideally zero but practically there exists a small dc o/p voltage known as o/p offset voltage.



{ To make this o/p voltage zero, a small voltage is required to be applied to one of the IIP terminals. Such a voltage makes the o/p exactly zero. This dc voltage, which makes the o/p voltage zero is called IIP offset voltage 'V_{ios}'. }

iv) Power supply voltage rejection ratio (PSRR) :-

PSRR is defined as the ratio of change in IIP offset voltage due to change in the supply voltage producing it, keeping other power supply voltage constant.

* If V_{EE} is constant & due to change in V_{cc}, there is change in IIP offset voltage then PSRR is expressed as.

$$\boxed{\text{PSRR} = \frac{\Delta V_{ios}}{\Delta V_{cc}} \Big|_{V_{EE} \text{ constant}}}$$

* If V_{cc} is constant & due to change in V_{EE}, there is change in IIP offset voltage then PSRR is expressed as

$$\boxed{\text{PSRR} = \frac{\Delta V_{ios}}{\Delta V_{cc}} \Big|_{V_{cc} \text{ constant}}}$$


(5)

v) I_P offset voltage :-

The dc voltage, which makes the o/p voltage zero, when the other terminal is grounded is called I_P offset voltage. It also depends upon temperature.

- * The ideal value of I_P offset voltage is zero but practically this value is small.


vii) I_P bias current :-

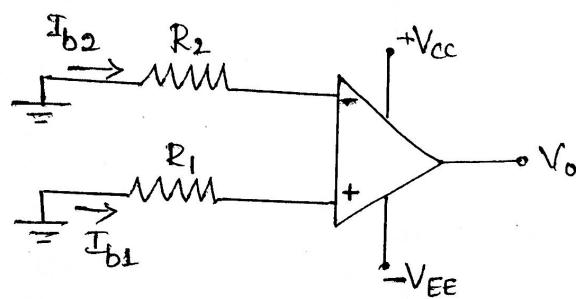

It is defined as the average value of the individual current flowing into the INV and Non-INV I_P terminals of the op-amp.

$$I_B = \frac{I_{b1} + I_{b2}}{2}$$

Open-loop amplifier :-

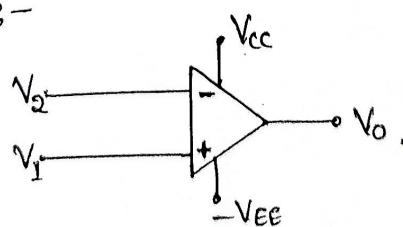

In open loop amplifier, there will be no feedback signal from o/p to I_P.
The o/p voltage is

$$V_o = A_{OL} (V_1 - V_2)$$

Closed Loop Amplifier :-

- * Explain why closed loop configuration of op-amp is used in all the practical amplifier circuit and bring out the advantages of closed loop operation with negative feedback.

June - 07, 6M

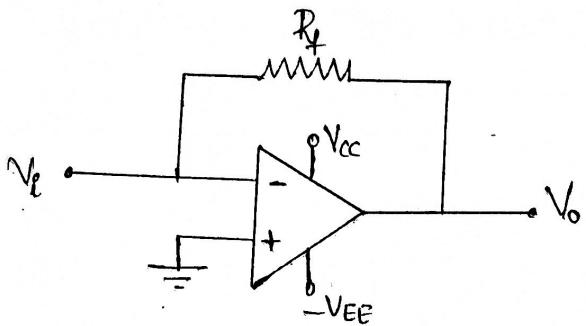


Fig: Op-amp with negative feedback.

- * The closed loop amplifier is possible using feedback i.e. feeding some part of the o/p back to the I/p through resistor. Always op-amp is used with negative feedback.

The gain resulting with feedback is called closed loop gain of the op-amp. Due to -ve feedback gain decreases.

Advantages of -ve feedback :-

- 1) It reduces the gain and makes it controllable.
- 2) It reduces the distortion.
- 3) It increases the bandwidth.
- 4) It increases the I/p resistance of the op-amp.
- 5) It decreases the o/p resistance of the op-amp.
- 6) It reduces the effects of temperature and power supply.

Op-amp Applications :-

(6)

The applications of op-amps are :-

- 1) Inverting amplifier.
- 2) Non-Inv amplifier.
- 3) Voltage follower.
- 4) Summer or Adder.
- 5) Subtractor or Difference amplifier.
- 6) Integrator etc.
- 7) Differentiator etc.

What is an op-amp ? Mention some of the applications
State the reason for its widespread applications.

June - 05, 8M

Op-amp is a directly coupled multistage voltage amplifier with high gain. It has ^{very} high IP impedance & a very low OP impedance.

Applications of op-amp :-

- 1) INV amplifier.
- 2) Non-INV amplifier
- 3) Voltage follower.
- 4) INV Summer.
- 5) Non-INV Summer
- 6) Difference or subtractor amplifier.
- 7) Integrator
- 8) Differentiator.

~~property of the op-amp.~~ capped at $\pm 12V$ due to saturable

NON-INVERTING amplifier :-

- * Draw the circuit diagram of a non-inverting summing amplifier and derive an equation for the output voltage.

June - 06, 8M

- * Show how an op-amp can be used of an Inverting and non-inverting amplifier. Derive the expression for their OIP voltages.

Jan - 03, 6M

- * List out the properties of an Ideal op-amp and with the circuit single. explain the significance of inverting & non-inverting IIP's.

Jan - 05, 8M.


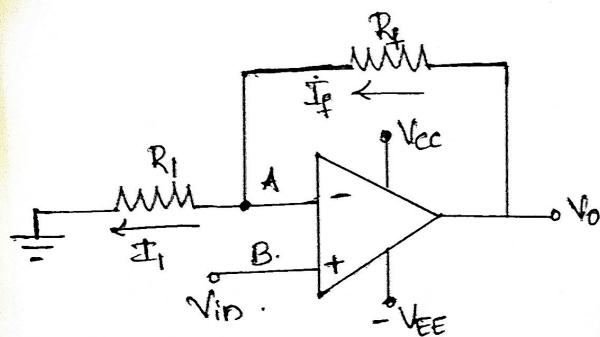


fig 1 @ : Non - INV amplifier.

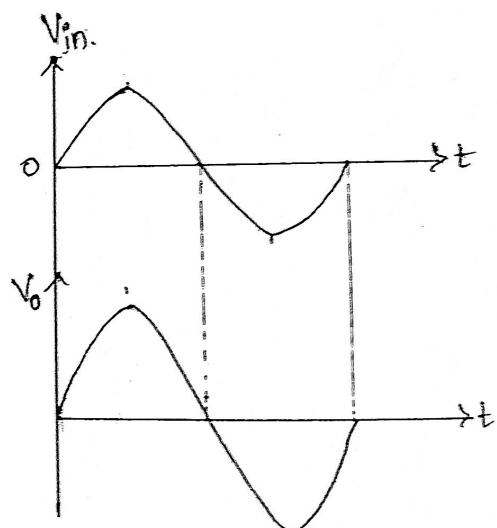

$$[R_1 \quad R_f]$$

- * In Non-INP amplifier, o/p voltage is amplified & is in-phase with the I/p signal.
- * The potential at node B is V_{in} , hence the potential at node A is same as node B i.e $\underline{V_A = V_B = V_{in}}$.

From I/p side, the current I is

$$I_i = \frac{V_A - 0}{R_1}$$

$$\boxed{I_i = \frac{V_{in}}{R_1}} \rightarrow \textcircled{1}$$

WKT $\boxed{V_A = V_{in}}$

From O/p side.

$$I_f = \frac{V_o - V_A}{R_f}$$

$$\boxed{I_f = \frac{V_o - V_{in}}{R_f}} \rightarrow \textcircled{2}$$

Equating eq \textcircled{1} & \textcircled{2}

$$\frac{V_{in}}{R_1} = \frac{V_o - V_{in}}{R_f}$$

$$\frac{V_{in}}{R_1} = \frac{V_o}{R_f} - \frac{V_{in}}{R_f}$$

$$\frac{V_o}{R_f} = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_f}$$

$$\frac{V_o}{R_f} = V_{in} \left[\frac{1}{R_1} + \frac{1}{R_f} \right]$$

$$\frac{V_o}{V_{in}} = R_f \left[\frac{R_f + R_1}{R_1 R_f} \right]$$

$$\frac{V_o}{V_{in}} = \left[\frac{R_f}{R_1} + \frac{R_1}{R_1} \right]$$

$$A = \left(1 + \frac{R_f}{R_1} \right)$$

O/p is in phase with I/p

(8)

$$\frac{V_o}{V_{in}} = \left(1 + \frac{R_f}{R_i} \right) \rightarrow ③$$

In eq ③, +ve sign indicates that the o/p is in-phase with the i/p.

* Draw the non-inverting voltage amplifier circuit using an op-amp and show that the closed loop voltage gain is given by.

$$A_{vf} = \frac{Av}{(1 + Av\beta)}$$

Av = open loop voltage gain of an op-amp.
 β = feedback factor.

July - 07, 6M

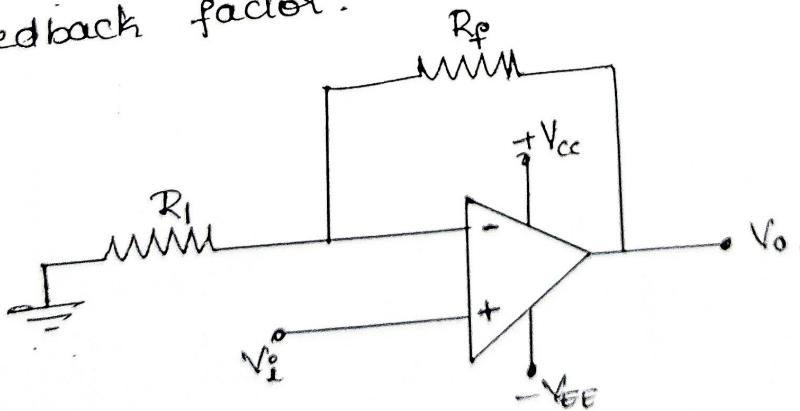


fig ① : Non-INV amplifier.

wrt Gain of the Non-INV amplifier is.

$$A_{vf} = \frac{V_o}{V_i} = \left(1 + \frac{R_f}{R_i} \right) \rightarrow ①$$

load gain $A_v = \infty$.

$$A_{Vf} = \frac{A_V}{(1 + A_V B)}$$

INVERTING AMPLIFIER :-

- * Show how op-amp can be used as an inverting amplifier ? Derive an expression for the voltage gain.

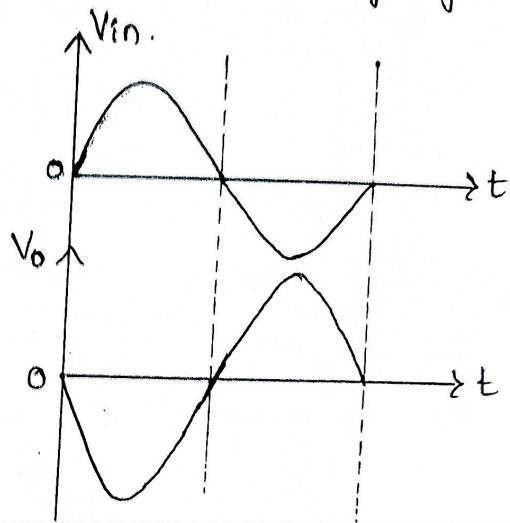
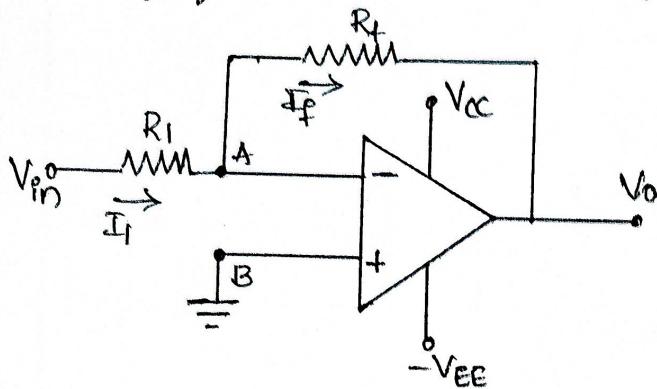


fig 1 @ : INV amplifier

(9)

In INV amplifier o/p voltage is amplified and 180° out of phase with respect to the I/P signal. By ground concept the potential at node A is also zero.

$$\therefore V_A = V_B = 0$$

From I/P side,

$$I_1 = \frac{V_{in} - V_A}{R_1} = \frac{V_{in} - 0}{R_1}$$

$$I_1 = \frac{V_o}{R_f} \rightarrow \textcircled{1}$$

From o/p side,

$$I_f = \frac{V_A - V_o}{R_f} = \frac{0 - V_o}{R_f}$$

$$I_f = -\frac{V_o}{R_f} \rightarrow \textcircled{2}$$

Equating eq \textcircled{1} & \textcircled{2} we get

$$\frac{V_{in}}{R_1} = -\frac{V_o}{R_f}$$

$$\frac{V_o}{R_f} = -\frac{V_{in}}{R_1}$$

$$\frac{V_o}{V_{in}} = -\left(\frac{R_f}{R_1}\right)$$

Where R_f/R_1 is closed loop gain & -ve sign. indicates that the polarity of o/p is opposite to that of I/P.

Voltage Follower

- * Explain how the Op-amp can be used as a voltage follower.

[Jan - 06, 41A.]

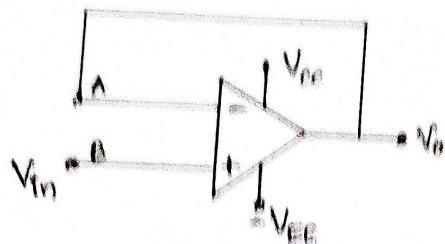


Fig 1 @ Voltage follower.

- * A circuit in which the op-amp follows.
- * Op-amp voltage is called voltage follower.
- * The potential at node B is V_o . Due to virtual ground concept the potential at node A is also V_o .

i.e.,
$$V_A = V_B = V_o$$

- * The node A is directly connected to op-amp terminal.

$$V_o = V_A$$

$$\therefore V_o = V_{in}$$

- * This circuit is also called source follower, unity gain amplifier buffer or isolation amplifier.

SUMMING or ADDER amplifier :-

- * With a neat diagram explain the working of an op-amp as summing amplifier.

[Jan - 10, 6M.]

When more than one op signal is applied to the INV or Non-INN amplifier, the op-amp performs addition of the applied op signals. Hence it is called summer or adder amplifier circuit.

10

INV Summer amplifier ckt :-

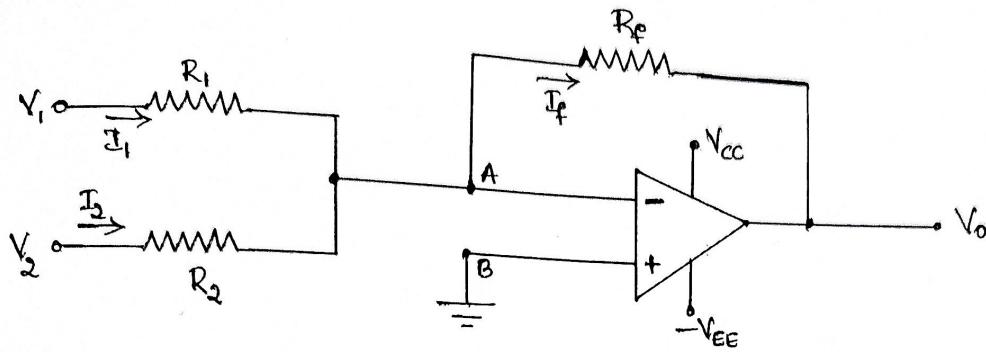


Fig ① : INV summing amplifier.

- * IIP signals which are to be added are applied to the INV IIP of op-amp.
 - * As node B is grounded, due to virtual ground concept the node A is also at ground potential ie. $V_A = V_B = 0$.
- From O/P side,

$$I_1 = \frac{V_1 - V_A}{R_1} = \frac{V_1 - 0}{R_1}$$

$I_1 = \frac{V_1}{R_1}$

 $\rightarrow ①$

$$I_2 = \frac{V_2 - V_A}{R_2} = \frac{V_2 - 0}{R_2}$$

$I_2 = \frac{V_2}{R_2}$

 $\rightarrow ②$

From O/P side,

$$I_f = \frac{V_A - V_0}{R_f} = \frac{0 - V_0}{R_f}$$

$I_f = -\frac{V_0}{R_f}$

 $\rightarrow ③$

Applying KCL at node A,

$$I_1 + I_2 - I_f = 0.$$

$$I_f = I_1 + I_2$$

Substituting eq ①, ② & ③ in eq ④, we get

$$-\frac{V_0}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V_0 = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} \right]$$

If $R_1 = R_2 = R_f = R$, then

$$V_0 = -R \left[\frac{V_1}{R} + \frac{V_2}{R} \right]$$

$$V_0 = -\frac{R}{R} [V_1 + V_2]$$

$$\boxed{V_0 = -[V_1 + V_2]}$$

From o/p side.

$$I = \frac{V_0 - V_A}{R_f}$$

$$\text{or } V_A = V_B.$$

$$I = \frac{V_0 - V_B}{R_f} \rightarrow \textcircled{6}$$

Equating eq. ⑤ & ⑥, we get

$$\frac{V_B}{R} = \frac{V_0 - V_f}{R_f}$$

$$\frac{V_B}{R} = \frac{V_0}{R_f} - \frac{V_B}{R_f}$$

$$\frac{V_B}{R} + \frac{V_f}{R_f} = \frac{V_0}{R_f}$$

$$V_B \left[\frac{1}{R} + \frac{1}{R_f} \right] = \frac{V_0}{R_f}$$

$$\frac{V_0}{R_f} = V_B \left[\frac{R + R_f}{RR_f} \right]$$

$$V_0 = V_B \left[\frac{R + R_f}{R} \right] \rightarrow \textcircled{7}$$

Substituting eq. ④ in eq. ⑦, we get

$$V_0 = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} \left[\frac{R + R_f}{R} \right]$$

If $R_1 = R_2 = R_f = R$

$$V_0 = \frac{V_1 R + V_2 R}{R + R} \left(\frac{R + R}{R} \right)$$

$$= R(V_1 + V_2) \cdot \frac{1}{R}$$

$$V_0 = V_1 + V_2$$

INTEGRATOR :-

Draw the circuit of op-amp as integrator and derive an expression for o/p voltage.

Jan-08, 6M

* Show with a circuit diagram how the op-amp can be used as an integrator.

July-09, 6M.

* Show with a deviation and circuit diagram, how an op-amp can be used as an integrator.

Jun-05, 6M.

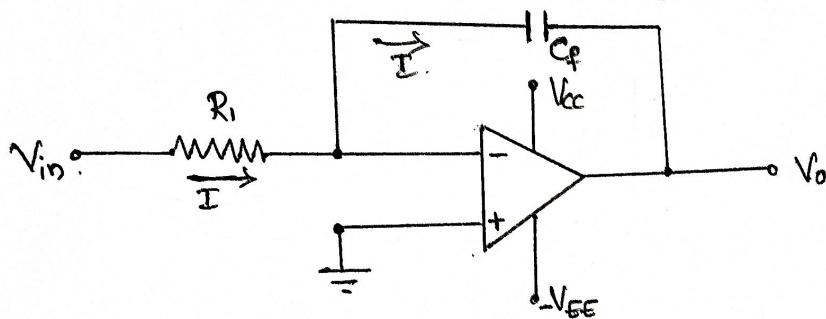


fig: op-amp as Integrator.

* In an Integrator ckt, the o/p voltage is the integration of the I/p voltage.

* From Virtual ground concept $V_A = V_B = 0$.

* As I/p current of op-amp is zero, the entire current I flows through R_1 , also flows through C_f .

From I/p side, we get

$$I = \frac{V_{in} - V_A}{R_1} = \frac{V_{in} - 0}{R_1}$$

$$\boxed{I = \frac{V_{in}}{R_1}} \rightarrow \textcircled{1}$$

From o/p side,

$$I = C_f \cdot \frac{d(V_A - V_o)}{dt}$$

$$I = C_f \cdot \frac{d(0 - V_o)}{dt}$$

$$I = -C_F \frac{dV_o}{dt} \rightarrow ②$$

Equating eq ① & ②, we get

$$\frac{V_{in}}{R_1} = -C_F \frac{dV_o}{dt}$$

Integrating both sides w.r.t. dt, we get

$$\int_0^t \frac{V_{in}}{R_1} dt = -C_F \int_0^t \frac{dV_o}{dt} \cdot dt$$

$$\int_0^t \frac{V_{in}}{R_1} dt = -C_F \cdot V_o.$$

$$V_o = -\frac{1}{R_1 C_F} \int_0^t V_{in} \cdot dt$$

Differentiator :-

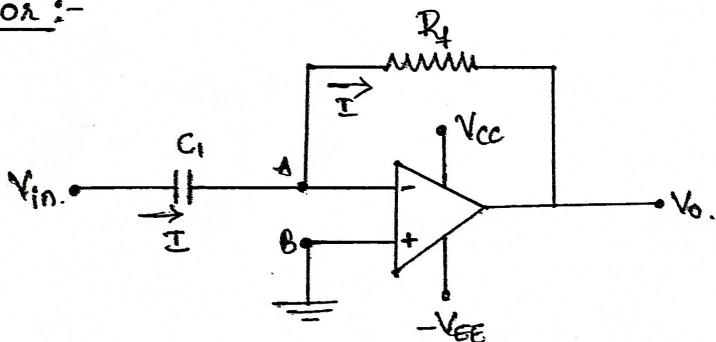


fig: op-amp as Differentiator.

- * The ckt which produces the differentiation of the IIP voltage at its o/p is called differentiator.
- * The node B is grounded. Due to virtual ground concept $V_A = V_B = 0$.
The IIP current of op-amp is zero, entire current I flows through the resistance R_F .

from IIP side,

$$I = C_1 \cdot \frac{d}{dt} (V_{in} - V_A)$$

$$I = C_1 \frac{d}{dt} V_{in} \rightarrow ①$$

as $V_A = 0$

from O/P side,

$$I = \frac{V_A - V_o}{R_f} = \frac{0 - V_o}{R_f}$$

$$I = -\frac{V_o}{R_f} \rightarrow ②$$

Equating eq ① & ②, we get

$$C_1 \frac{dV_{in}}{dt} = -\frac{V_o}{R_f}$$

$$V_o = -R_f C_1 \cdot \frac{dV_{in}}{dt} \rightarrow ③$$

- * The eq ③ shows that the O/P is $R_f C_1$ times the differentiation of the IIP & product $R_f C_1$ is called time constant of the differentiator.

SUBTRACTOR or DIFFERENCE amplifier :-

(Not in syllabus)

- * Show that the op-amp circuit shown below can work as a subtractor.
- * Explain how an op-amp can be used as subtract. Obtain an expression for its o/p.

July-04, 3M	July 05, 5M
-------------	-------------

July, 04 + 5M
